


Assignment Project Exam Help

Add WeChat powcoder

# L8\_1 Floating-Point Arithmetic

EECS 370 – Introduction to Computer Organization – Fall 2020



# Assignment Project Exam Help

# Learning Objectives

Add WeChat powcoder

- To understand the algorithm for arithmetic operations using IEEE 754 floating-point values.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Floating Point Representation

Floating  
Point  
Review

$10.625_{10} \Rightarrow 1010.101_2$


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

$1.010101 \times 2^3$

This must be a 1!  
So don't store it.

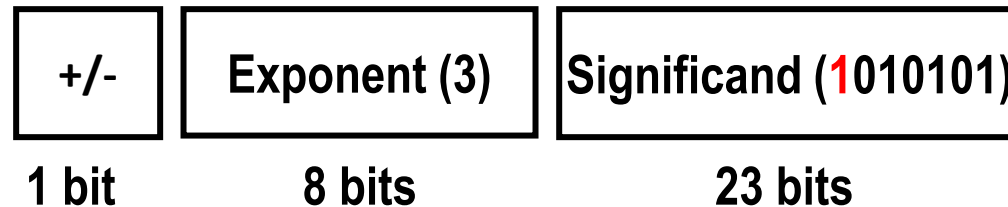

$10.625_{10} = 0 \ 10000010 \ 01010100000000000000000_2$

# Floating Point - Example

Floating  
Point

Problem: What is the value (in decimal) of the following IEEE 754 floating point encoded number?

1	10000101	010110010000000000000000
---	----------	--------------------------

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

sign bit	1	- (negative)
----------	---	--------------

exponent	10000101	$133 - 127 = 6$ (biased by 127)
----------	----------	---------------------------------

significand	010110010000000000000000	add implicit 1
-------------	--------------------------	----------------

$-1.01011001 \times 2^6$	shift radix point 6 places	$-1010110.01$
--------------------------	----------------------------	---------------

$$-1010110.01 = -(2^6 + 2^4 + 2^2 + 2^1 + 2^{-2}) = -(64 + 16 + 4 + 2 + \frac{1}{2}) = -86.25_{10}$$

# Floating Point Multiply - Example

Floating  
Point

**10.625** <sub>10</sub>

**10** <sub>10</sub>

Algorithm:

1. Convert to binary
2. Convert binary numbers to IEEE 754 floating-point
3. Multiply
  1. Sign bit - xor
  2. Add exponents - *mind the bias! (127)*
  3. Multiply significands

# Floating Point Multiply - Example

Floating Point

$$10.625_{10} = 1010.101_2 \quad \Rightarrow \quad \begin{array}{c|c|c} 0 & 10000010 & 010101000000000000000000 \\ \hline 0 & 10000010 & 010000000000000000000000 \end{array}$$

Assignment Project Exam Help  
Add WeChat powcoder  
<https://powcoder.com>

$$\begin{array}{r} 1010101 \\ \times 101 \\ \hline 1010101 \\ 0000000 \\ 1010101 \\ \hline 110101001 \end{array}$$

$$\begin{array}{c|c|c} 0 & 10000010 & 010101000000000000000000 \\ \hline 0 & 10000010 & 010000000000000000000000 \\ \hline 0 & 10000010 & 010101001000000000000000 \end{array}$$

$$1101010.01_2 = 106.25_{10}$$

# Floating Point Addition



- More complicated than floating point multiplication!
- If exponents are unequal, must shift the significand of the smaller number to the right to align the corresponding place values
- Once numbers are aligned, simple addition (could be subtraction, if one of the numbers is negative)
- Renormalize (shift to get back into proper "scientific notation")
- Added complication: rounding to the correct number of bits to store could denormalize the number, and require one more step

# Floating Point Addition

1. Shift smaller exponent right to match larger.
2. Add significands
3. Normalize and update exponent
4. Check for "out of range"


Normalize: shift significand (mantissa) for integer part to be 1 and remaining bits are fractions

Example:  
 $1010.101_2$   
Normalized is  
 $1.010101 \times 2^3$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

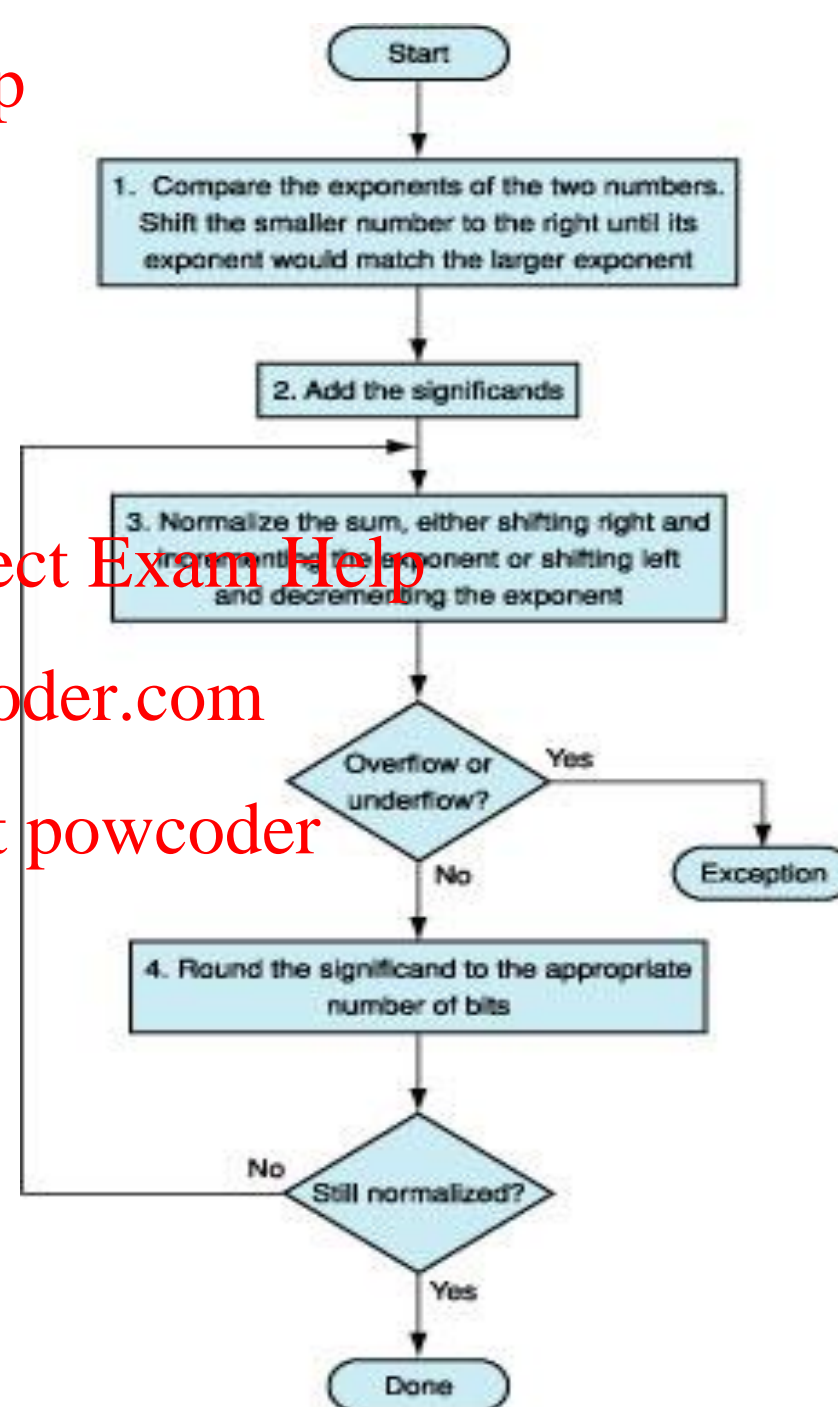

Floating Point



# Floating Point Addition - Example

Floating  
Point

Problem: Add two numbers using IEEE floating point addition: **101.125 + 13.75**

1. Convert to IEEE 754 format
2. Shift smaller exponent right to match larger.
3. Add significands
4. Normalize and update exponent
5. Check for "out of range"

# Floating Point Addition - Example

Floating Point

Problem: Add two numbers using IEEE floating point addition: **101.125 + 13.75**

101.125      0 10000101 100101001000000000000000

13.75      0 10000010 101110000000000000000000

<https://powcoder.com>

Shift by 6 - 3 = 3

Shift mantissa by difference in exponent

Add WeChat powcoder

13.75      0 10000101 001101110000000000000000

0 10000101 110010111000000000000000

Sum Significands

1 1 0 0 1 0 1 0 0 1  
+ 0 0 0 1 1 0 1 1 1 0  
-----  
1 1 1 0 0 1 0 1 1 1

Sum didn't overflow, so  
no re-normalization  
needed

$$= 1.110010111_2 \times 2^6 = 114.875_{10}$$

# Assignment Project Exam Help

## More Precision and Range


Add WeChat powcoder



- We have described IEEE-754 binary32 floating point format, commonly known as “single precision” (“float” in C/C++)
  - 24 bits precision; equivalent to about 7 decimal digits
  - $3.4 * 10^{38}$  maximum value
  - Good enough for many but not all calculations
- IEEE-754 also defines a larger binary64 format, “double precision” (double data type in C/C++)
  - 53 bits precision, equivalent to about 16 decimal digits
  - $1.8 * 10^{308}$  maximum value
  - Most accurate physical values currently known only to about 47 bits precision, about 14 decimal digits

# Floating Point Precision

Floating  
Point

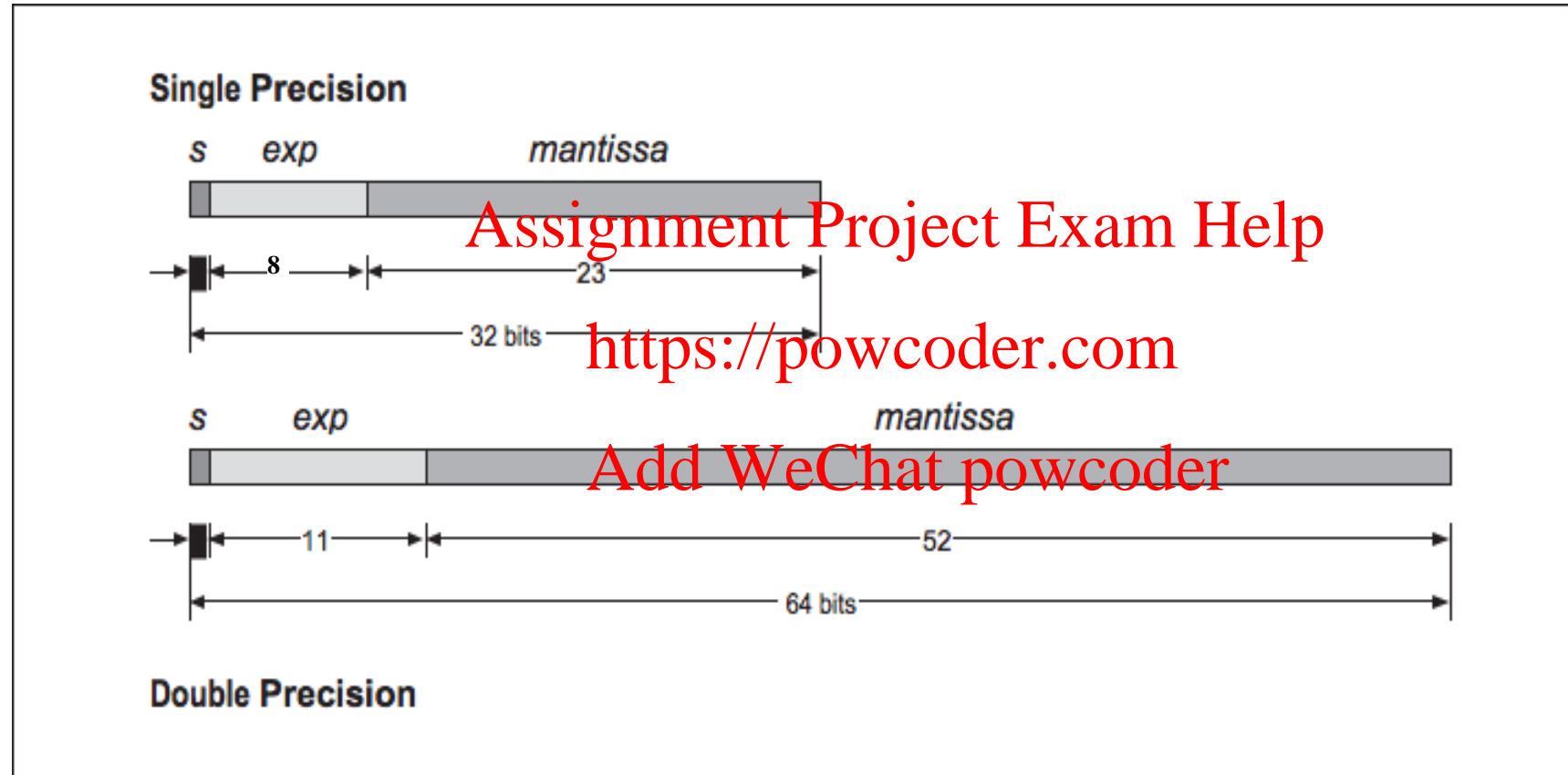

# Logistics

## Assignment Project Exam Help

Add WeChat powcoder

- There are 3 videos for lecture 8
  - L8\_1 – IEEE\_Floating-Point\_Arithmetic
  - L8\_2 – Basic-Electronics-Logic\_Gates
  - L8\_3 – Combinational-Logic
- There is one worksheet for lecture 8
  - 1. Logic gates – complete at the end of all 3 videos.

<https://powcoder.com>


Add WeChat powcoder

Assignment Project Exam Help

Add WeChat powcoder

# L8\_2 Basic-Electronics\_Logic-Gates

EECS 370 – Introduction to Computer Organization – Fall 2020



# Office Hours

Assignment Project Exam Help  
Add WeChat powcoder

- Drop by office hours, ask questions, say ‘hi’
- Just in case you did not see them on the calendar:  
Assignment Project Exam Help  
Tuesdays 11am to 12 noon (EST) – individual meetings

<https://powcoder.com>


Group office hours Add WeChat powcoder

Tuesdays 4pm to 4:30 pm

Thursdays 9:45 am to 10:15 am

Thursdays 2:30 pm to 3:00 pm

<https://umich.zoom.us/j/92153246345>



# Assignment Project Exam Help

## Learning Objectives

Add WeChat powcoder

- To identify logic gates used in combinational logic circuits and describe their operations.
- Be able to create the functionality of any logic gate with the NOR gate, (and therefore, the nor instruction in LC-2K).

<https://powcoder.com>

Add WeChat powcoder





# Assignment Project Exam Help

## Levels of Abstraction

Add WeChat powcoder

- Quantum level, solid state physics
- Conductors, Insulators, Semiconductors
- Doping silicon to make diodes and transistors
- Simple gates, Boolean logic, and truth tables
- Combinational logic: muxes, decoders
- Clocks
- Sequential logic: latches, memory
- State machines
- Processor Control: Machine instructions
- Computer Architecture: Defining a set of instructions

# Start with the Materials: Conductors and Insulators

Add WeChat powcoder

- **Conductor**: a material that permits electrical current to flow easily. (low resistance to current flow)
  - Lattice of atoms with free electrons
- **Insulator**: a material that is a poor conductor of electrical current (High resistance to current flow)
  - Lattice of atoms with strongly held electrons
- **Semi-conductor**: a material that can switch between an (okay) conductor and an (okay) insulator
  - Controlled via an external voltage
  - Basis for "logical switches" that make up digital circuits


Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder
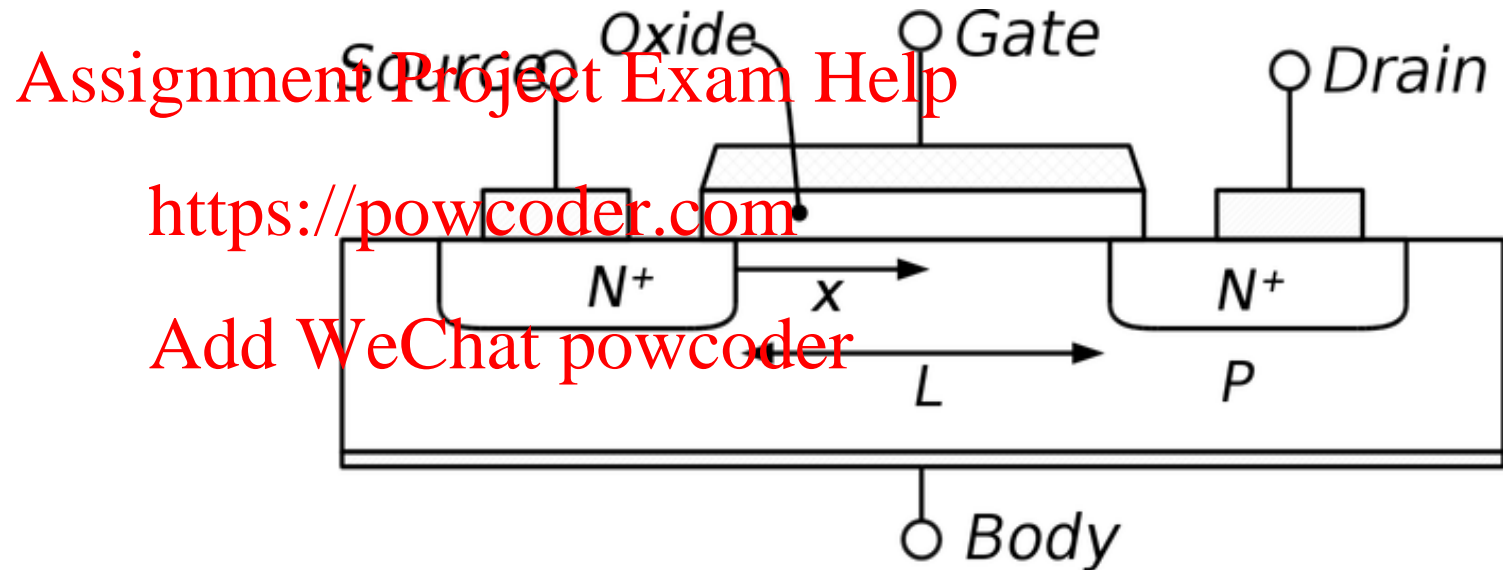
# Making a Transistor

- Our first level of abstraction is the transistor (basically 2 diodes sitting back-to-back)




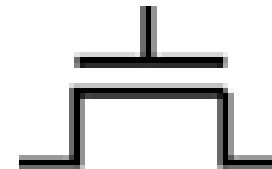- Electrical engineers use a symbol like this:



# Recent Pictures and the Near Future

Source: Intel

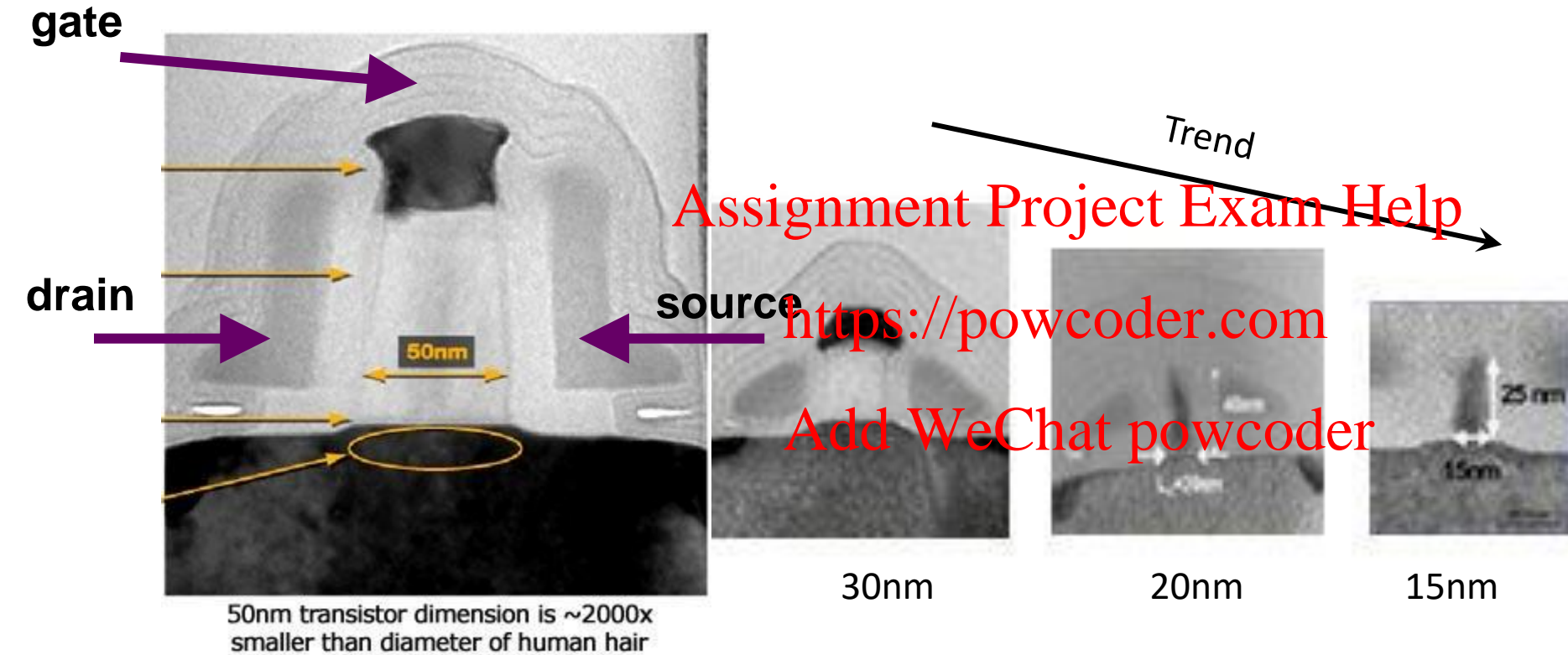

90nm technology	65nm technology	45nm technology	32nm technology	14nm technology	7nm technology	5nm technology
2003	2005	2008	2010	2014	2018	2020




# Assignment Project Exam Help
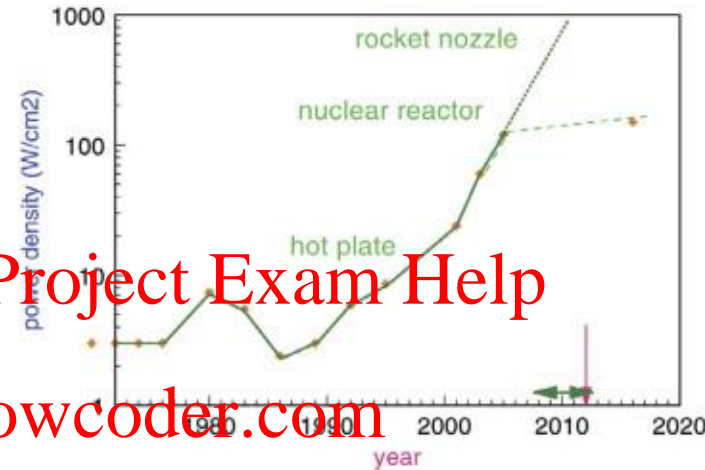
## Present and Future Problems


Add WeChat powcoder

- Area is the least of them
- Power density – Watts/mm<sup>2</sup>
- Leakage current





<https://powcoder.com>

- Reliability (faults)

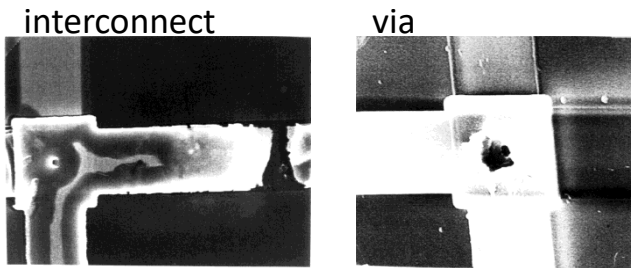

Add WeChat powcoder

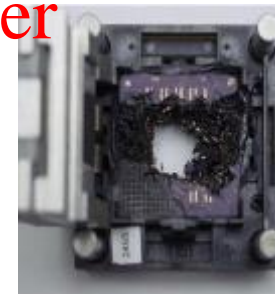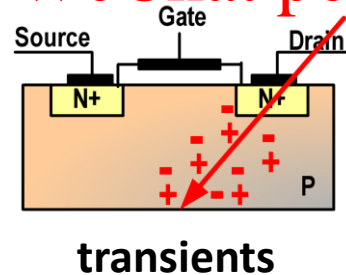

Testing burn-in


- Process variation (not all transistors are equal)



# Assignment Project Exam Help

## As for power: Cooking-aware Computing

Add WeChat powcoder

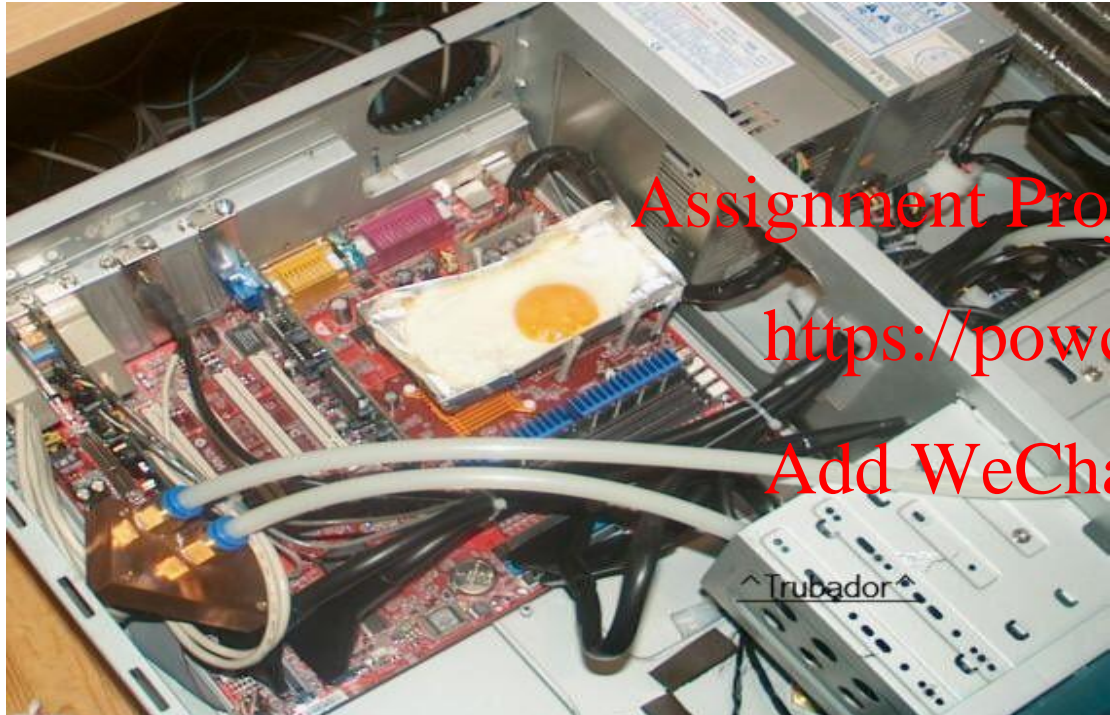

Source: The New York Times, 25 June 2002



Liquid Nitrogen Cooling

# Assignment Project Exam Help

## Basic Gate: Inverter


Add WeChat powcoder

**CS abstraction**  
**- logic function**

Truth Table

I	O
0	1
1	0

**Schematic symbol (CS/EE)**

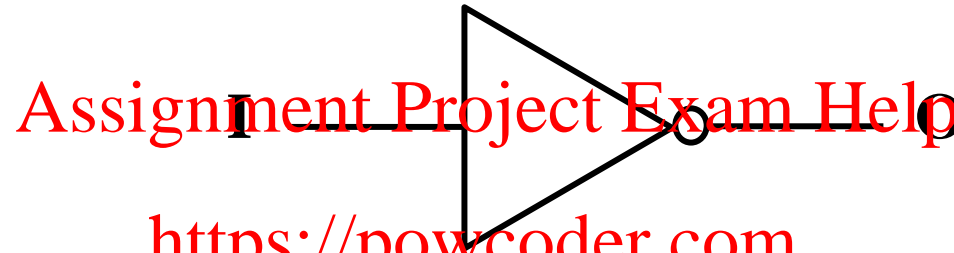

Add WeChat powcoder



# Assignment Project Exam Help

## Basic Gate: NAND

Add WeChat powcoder

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder




# Assignment Project Exam Help

## Basic Gates: AND, OR, XOR

Add WeChat powcoder

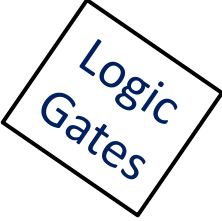


### AND

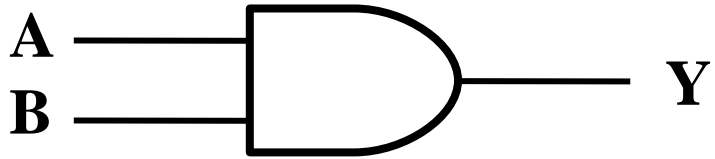

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


### OR

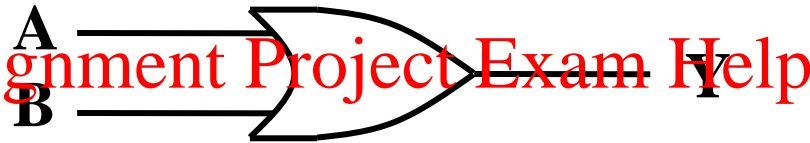

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

### XOR

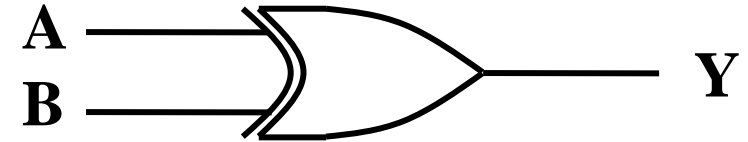

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

# Assignment Project Exam Help

## Basic Gates: NOR

Add WeChat powcoder

### NOR

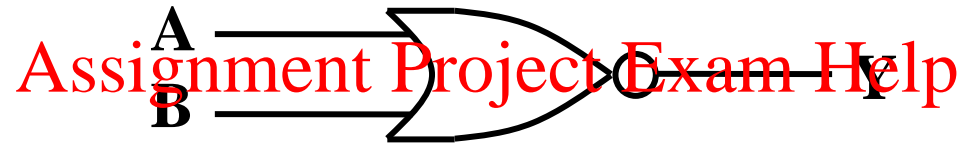

<https://powcoder.com>

Truth Table


Add WeChat powcoder

A	B	$A \mid B$	Y
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

# Assignment Project Exam Help

## Logic Gate Exercise

Add WeChat powcoder

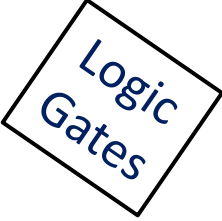

- NOR is logically complete
  - This means that all gates can be implemented using only NORs
    - All gates can be implemented in LC2K
  - NAND is also logically complete
- Exercise:
  - Implement INV using only NOR gates
  - Implement AND using only NOR gates
  - Implement OR using only NOR gates
  - Hint Demorgan's Law:
    - $A \mid\mid B = !( !A \&\& !B )$
    - $!(A \mid\mid B) = !A \&\& !B$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


# Assignment Project Exam Help

## Logic Gate Exercise – INV (!) using NOR

Add WeChat powcoder

### NOR



$!(A \ || \ B) = A \ \text{NOR} \ B$   
 substitute A for B  
 $!(A \ || \ A) = A \ \text{NOR} \ A$   
 $!(A) = A \ \text{NOR} \ A$   
 $!A = A \ \text{NOR} \ A$

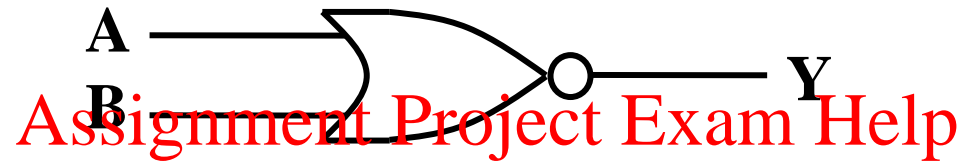

<https://powcoder.com>

Add WeChat powcoder

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

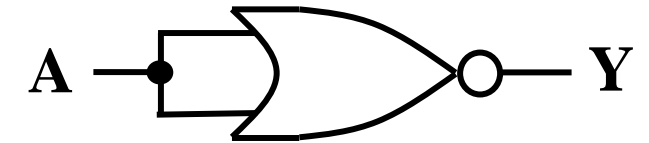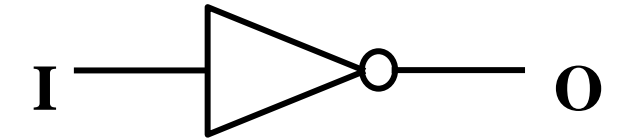

Truth Table

I	O
0	1
1	0

# Assignment Project Exam Help

## Logic Gate Exercise – AND using NOR

Add WeChat powcoder


$$\neg(A \vee B) = \neg A \wedge \neg B = A \text{ NOR } B$$

$$\neg A \text{ NOR } \neg B = A \wedge B$$

substitute A NOR A for !A

substitute B NOR B for !B
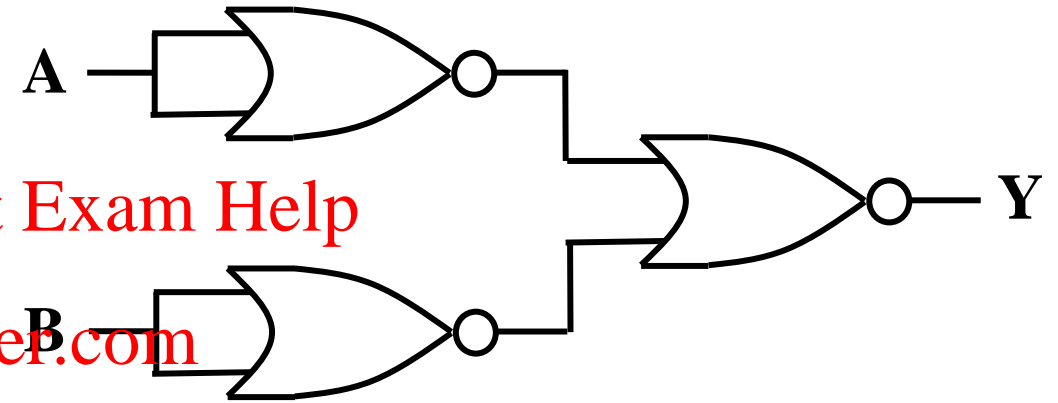
$$A \wedge B = (A \text{ NOR } A) \text{ NOR } (B \text{ NOR } B)$$



Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


A	B	A && B	Y
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

# Assignment Project Exam Help


## Logic Gate Exercise – OR using NOR

Add WeChat powcoder

**NOR**

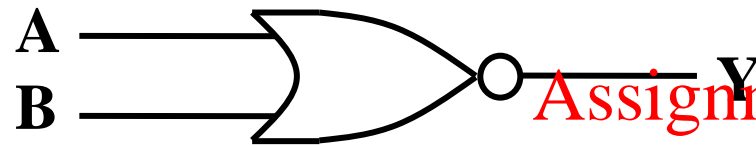

**OR**

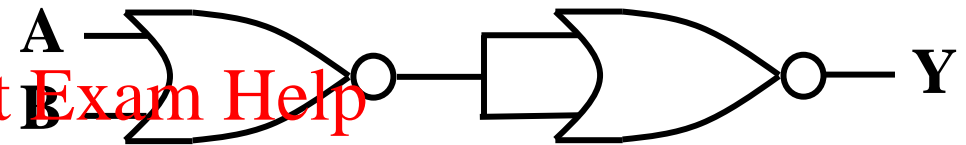

Truth Table

<https://powcoder.com>

A	B	$A \mid B$	Y	$\neg Y$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	0	1

# Logistics

## Assignment Project Exam Help

Add WeChat powcoder

- There are 3 videos for lecture 8
  - L8\_1 – IEEE\_Floating-Point\_Arithmetic
  - L8\_2 – Basic-Electronics-Logic Gates
  - L8\_3 – Combinational-Logic
- There is one worksheet for lecture 8
  - 1. Logic gates – complete at the end of all 3 videos.

<https://powcoder.com>

Add WeChat powcoder



Assignment Project Exam Help

Add WeChat powcoder




# L8\_3 Combinational-Logic

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder



# Assignment Project Exam Help

# Learning Objectives

Add WeChat powcoder

- To create circuits using combinations of basic gates.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Assignment Project Exam Help

## Building Complexity: Addition (1)

Add WeChat powcoder

GOAL: We want to design a circuit that performs binary addition

Let us start by adding two bits

- Design a circuit that takes two bits as input (A and B)
- Generates a sum and carry bit (S and C)

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


	0	1	1	0
	1	0	1	1
+	0	0	1	1
	1	1	1	0
	1	1	1	0
	1	1	1	0

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

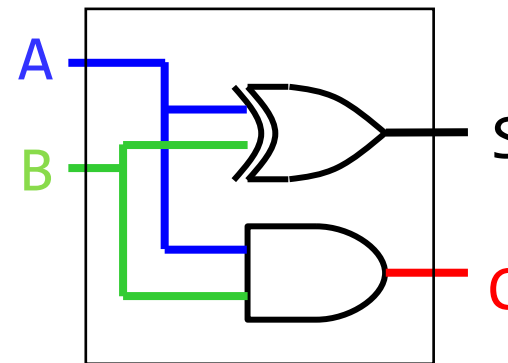1. Make a truth table
2. Design a circuit



Half-Adder

# Assignment Project Exam Help

## Building Complexity: Addition (1)


Add WeChat powcoder

$$\begin{array}{r}
 0\ 1\ 1\ 0 \\
 1\ 0\ 0\ 1\ 1 \\
 +\ 0\ 0\ 1\ 1\ 0 \\
 \hline
 1\ 1\ 0\ 0\ 1
 \end{array}$$

Comb.  
Logic


- Now we can add two bits, but how do we deal with carry bits?
  - We must design a circuit that can add three bits
    - Inputs: A, B, Cin
    - Outputs: S, Cout
- 1. Design a truth table
- 2. Circuit
- How do we combine these?

<https://powcoder.com>

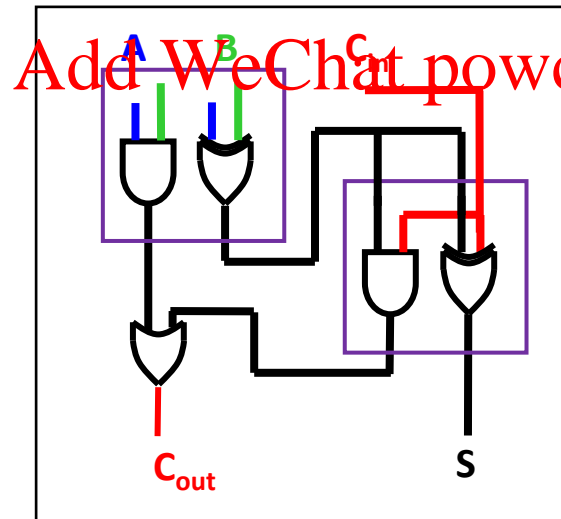

Cin	A	B	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# 8-bit Ripple Carry Adder

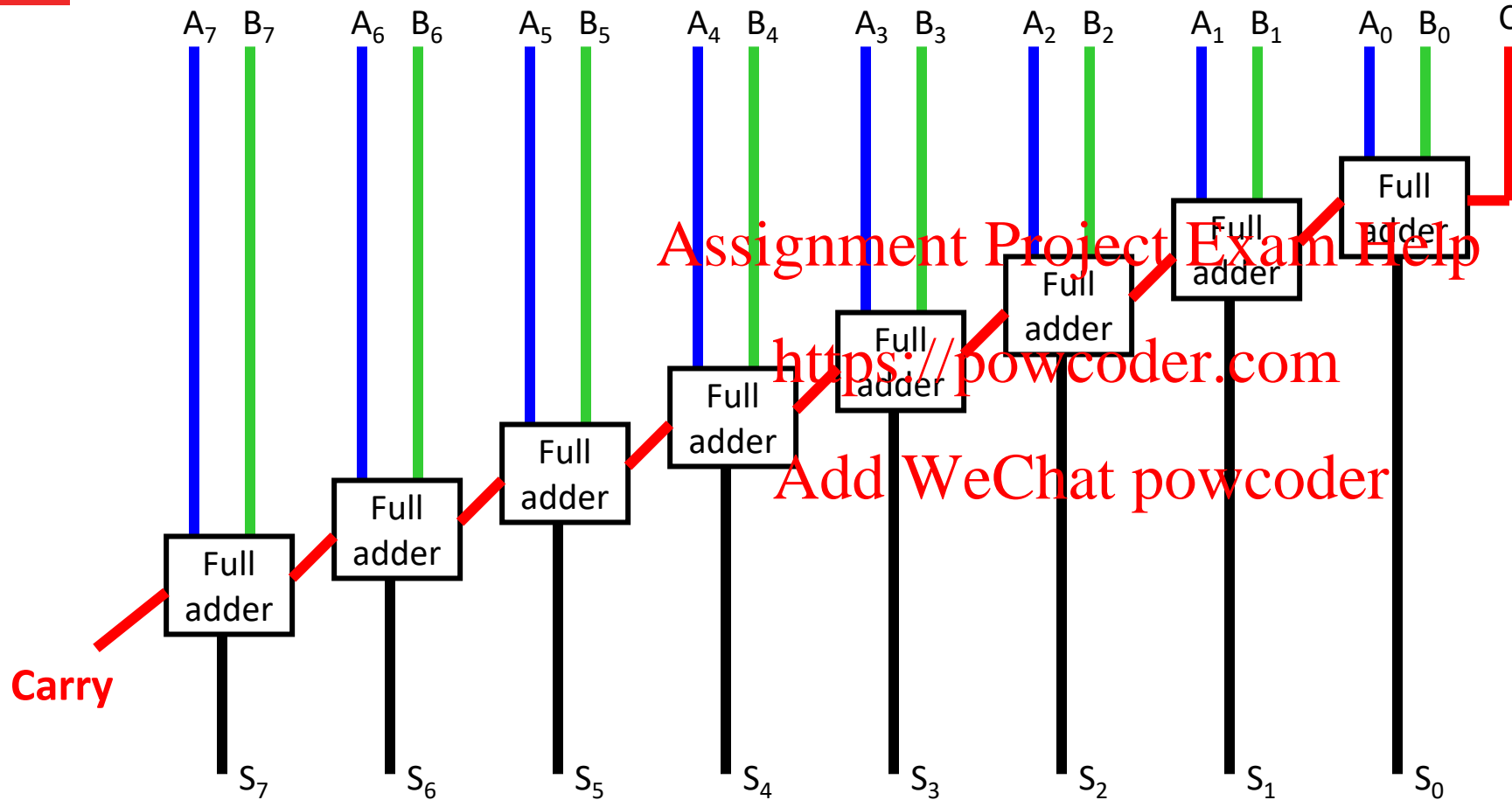

*Unfortunately, this has a very large propagation time for 32 or 64 bit adds*

# Building Complexity: Selecting

Assignment Project Exam Help

Add WeChat powcoder



- We want to design a circuit that can select between two inputs - Let us start with a one-bit version

A	B	S	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Draw a truth table

Assignment Project Exam Help

<https://powcoder.com>

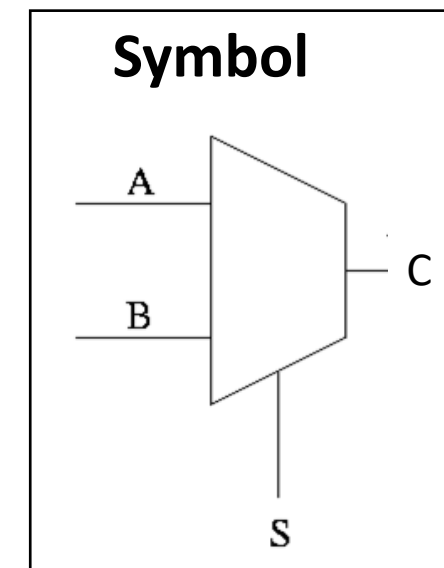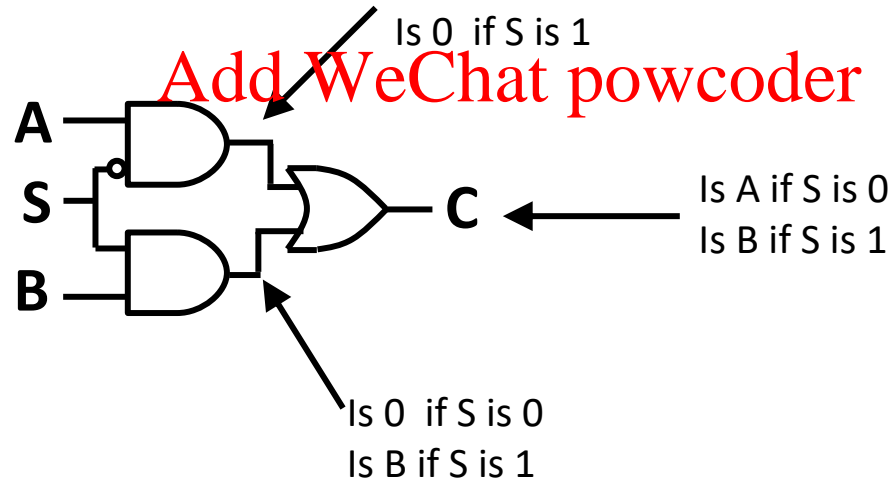


Multiplexer (Mux)

Comb. Logic

# Multiplexer - Example

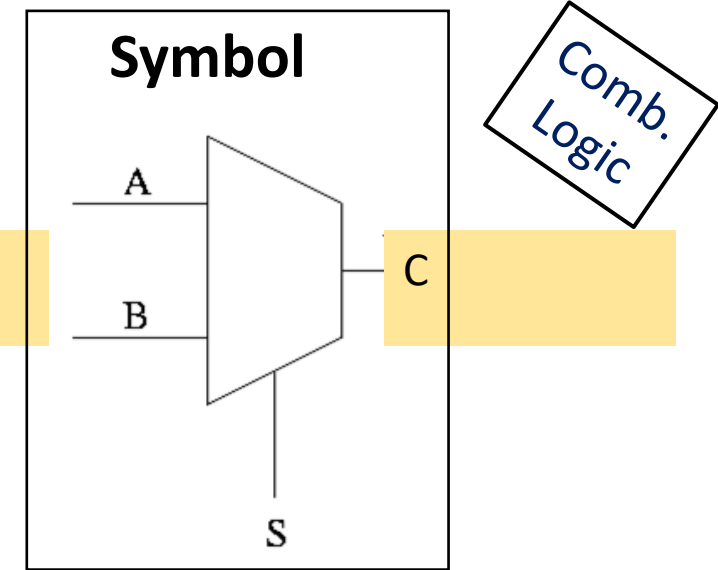Problem: Build a 4x1 mux using only 2x1 muxes





Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Multiplexer - Example

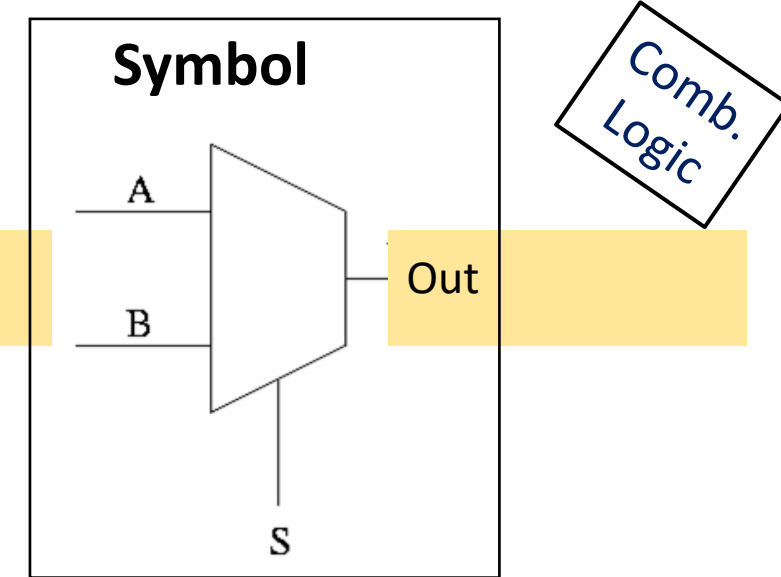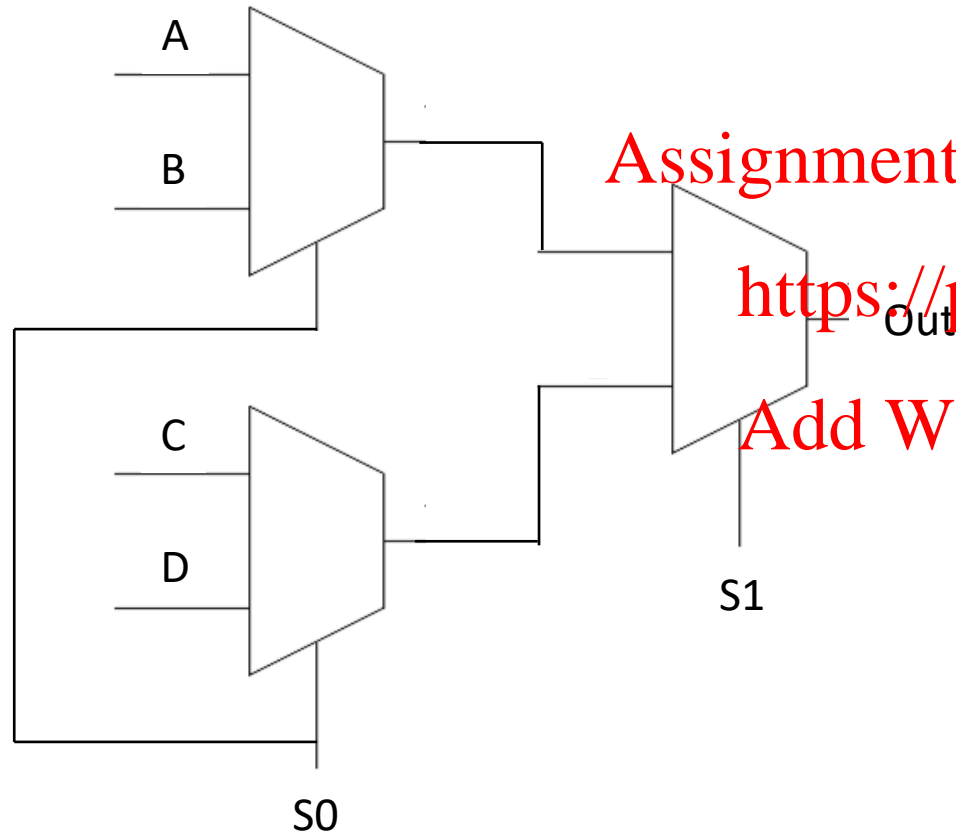Problem: Build a 4x1 mux using only 2x1 muxes



S1	S0	Out
0	0	A
0	1	B
1	0	C
1	1	D



# Assignment Project Exam Help


## Building Complexity: Decoding

Add WeChat powcoder

- Another common device is a decoder
  - Input: N-bit binary number
  - Output:  $2^N$  bits, exactly one of which will be high

<https://powcoder.com>

Add WeChat powcoder

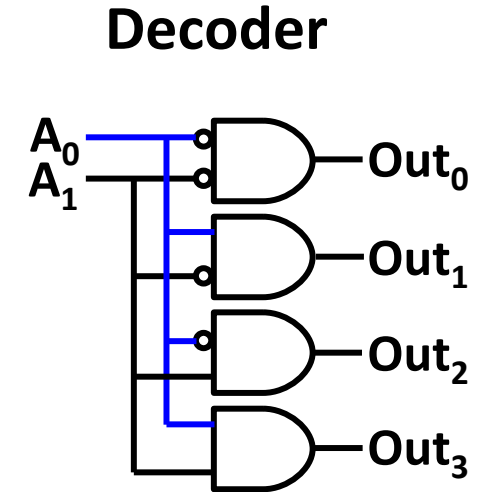

# Assignment Project Exam Help

## Combinational Circuits Implement Boolean Expressions

Add WeChat powcoder


- Output is determined exclusively by the input
- No memory: Output is valid only as long as input is
  - Adder is the basic gate of the ALU (Future lecture)
  - Decoder is the basic gate of indexing
  - MUX is the basic gate controlling data movement

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder


Half-Adder

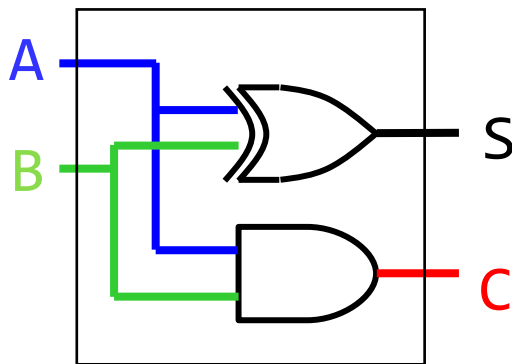

Decoder

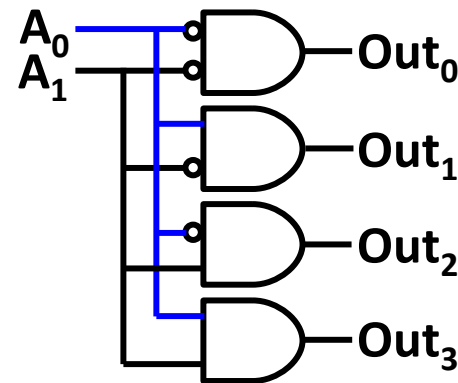

Mux

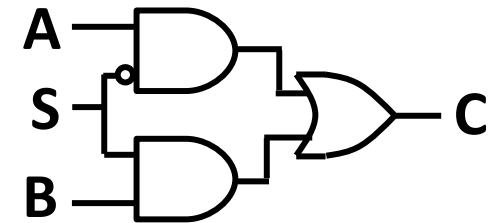



# Logistics

## Assignment Project Exam Help

Add WeChat powcoder

- There are 3 videos for lecture 8
  - L8\_1 – IEEE\_Floating-Point\_Arithmetic
  - L8\_2 – Basic-Electronics-Logic\_Gates
  - L8\_3 – Combinational-Logic
- There is one worksheet for lecture 8
  - 1. Logic gates – complete at the end of all 3 videos.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder